

**Introduction to Programming and
Personal Computing**

Boolean Algebra, Logic Gates, and Truth Tables

AND

--	--	--

OR

--	--	--

**Introduction to Programming and
Personal Computing**

NOT

--	--	--

Exclusive OR


--	--	--

NAND

--	--	--

Exercises:

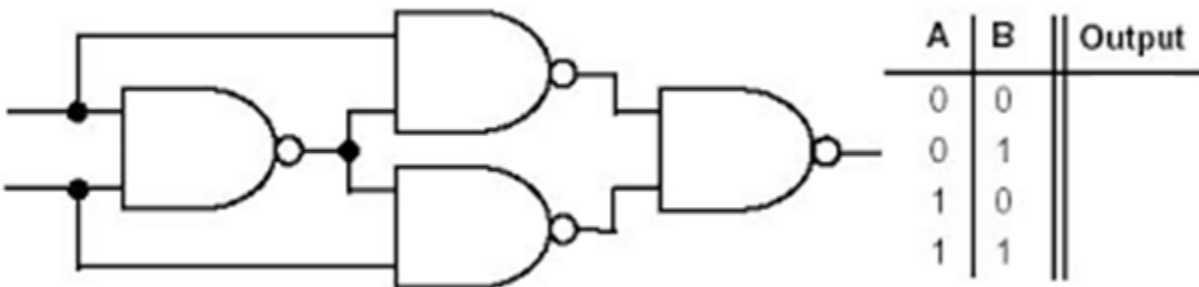1) Create a truth table and identify the function of the following circuit:



2) Create a truth table and identify the function of the following circuit:

